

# Department of Electronics & Communication Engineering

(Faculty of Technology, Dharmsinh Desai University, Nadiad)

Academic Year: 2022 - 2023

## TUTORIAL – 10

**Subject** : *PHYSICS (Module-5 & 6)*

**Class** : *B. Tech. Sem.II (EC/IT)*

### Q.1 Select the most appropriate option.

- (1) An oscillator always needs an amplifier with \_\_\_\_\_  
(I) Negative feedback (II) Positive feedback (III) Both types of feedback  
(IV) No feedback required
- (2) The voltage that starts an oscillator is caused by \_\_\_\_\_  
(I) Ripple from the power supply  
(II) Thermal noise voltage in electronic component  
(III) The input signal from a generator  
(IV) Positive feedback
- (3) For oscillations to start in a circuit, the loop gain must be greater than 1 when the phase shift around the loop is \_\_\_\_\_  
(I)  $90^\circ$  (II)  $180^\circ$  (III)  $270^\circ$  (IV)  $360^\circ$
- (4) A D-MOSFET can operate in the \_\_\_\_\_  
(I) Depletion-mode only (II) Enhancement-mode only  
(III) Depletion-mode or enhancement-mode (IV) Low-impedance mode
- (5) The voltage that turns on an Enhancement- MOSFET device is the \_\_\_\_\_  
(I) Gate-source cutoff voltage (II) Pinchoff voltage  
(III) Threshold voltage (IV) Knee voltage
- (6) MOSFET is \_\_\_\_\_ controlled constant \_\_\_\_\_ source.  
(I) current, current (II) voltage, current  
(III) current, voltage (IV) voltage, voltage

### Q.2 Do as Directed (Descriptive Answers, Examples etc)

- (1) State the criteria(s) to build up the oscillations in the oscillator circuit.
- (2) Draw the block diagram of oscillator and explain working of the same in brief.
- (3) An n-channel D-MOSFET has the specifications  $V_{GS(off)} = -2\text{ V}$  and  $I_{DSS} = 4\text{ mA}$ . Given  $V_{GS}$  values of  $-0.5\text{ V}$ ,  $-1.0\text{ V}$ ,  $-1.5\text{ V}$ ,  $+0.5\text{ V}$ ,  $+1.0\text{ V}$ , and  $+1.5\text{ V}$ , determine  $I_D$ .
- (4) Calculate  $R_{DS(on)}$  for the E-MOSFET having  $V_{DS(on)} = 0.25\text{ V}$  and  $I_{D(on)} = 45\text{ mA}$ .
- (5) An E-MOSFET has  $R_{DS(on)} = 2\ \Omega$  when  $V_{GS(on)} = 3\text{ V}$  and  $I_{D(on)} = 500\text{ mA}$ . If it is biased in the ohmic region, what is the voltage across it for each of these drain currents:  
(a)  $I_{D(sat)} = 25\text{ mA}$  (b)  $I_{D(sat)} = 50\text{ mA}$  (c)  $I_{D(sat)} = 100\text{ mA}$  (d)  $I_{D(sat)} = 200$